


ES204 Digital Systems

Implementation of Tiny Processor

Abhinav Khot (23110006)

Arjun B Dikshit (23110040)

## Block diagram of workflow:

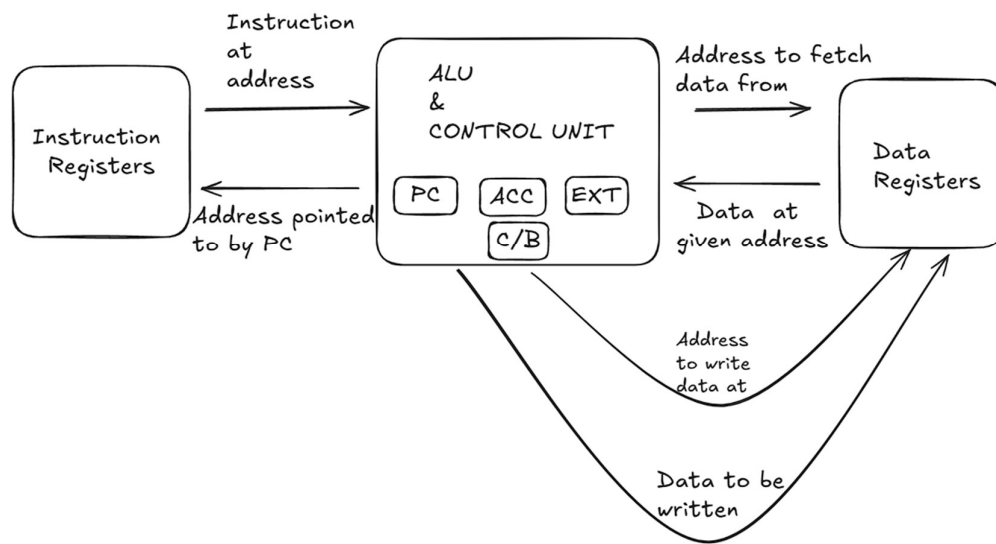

As soon as the program counter is updated, the new instruction is fetched from the instruction register and according to the instruction any required data is fetched from the data register. The required computation is done and the **next** value of PC, EXT, ACC, C/B and the data that needs to be written onto the data register is stored. In the next clock edge, the registers are updated with the new values and the PC is updated.

## Simulation Results:

**Execute ALL Instructions:**




### Sample Program:

We write a program for an if-else statement. The program essentially loads a value from a register\_0 into the ACC and checks if the new ACC value is greater than or equal to value in register\_1. If it is the case then we set ACC to the value of register\_1 else we decrement ACC.


Data registers are set such that IF block is executed:





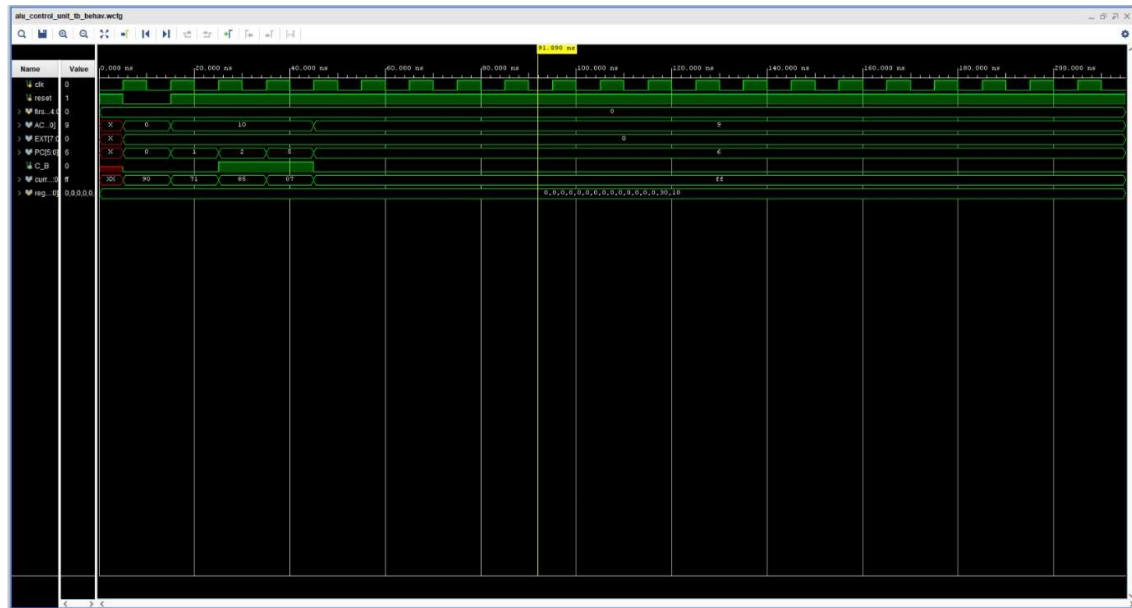Data registers are set such that ELSE block is executed:



### RTL Analysis Schematic:

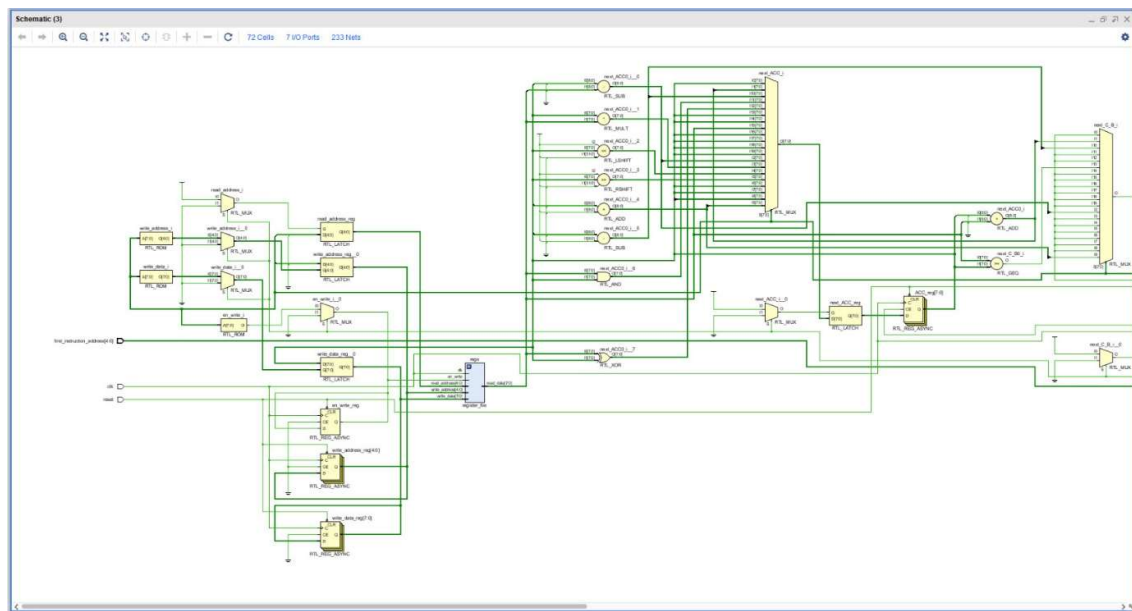

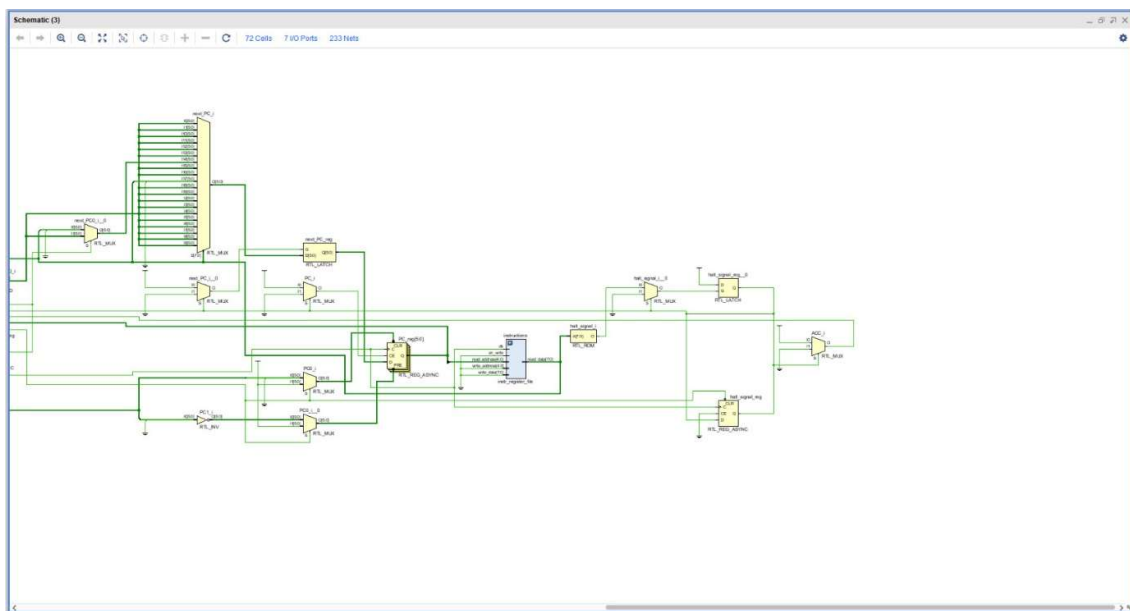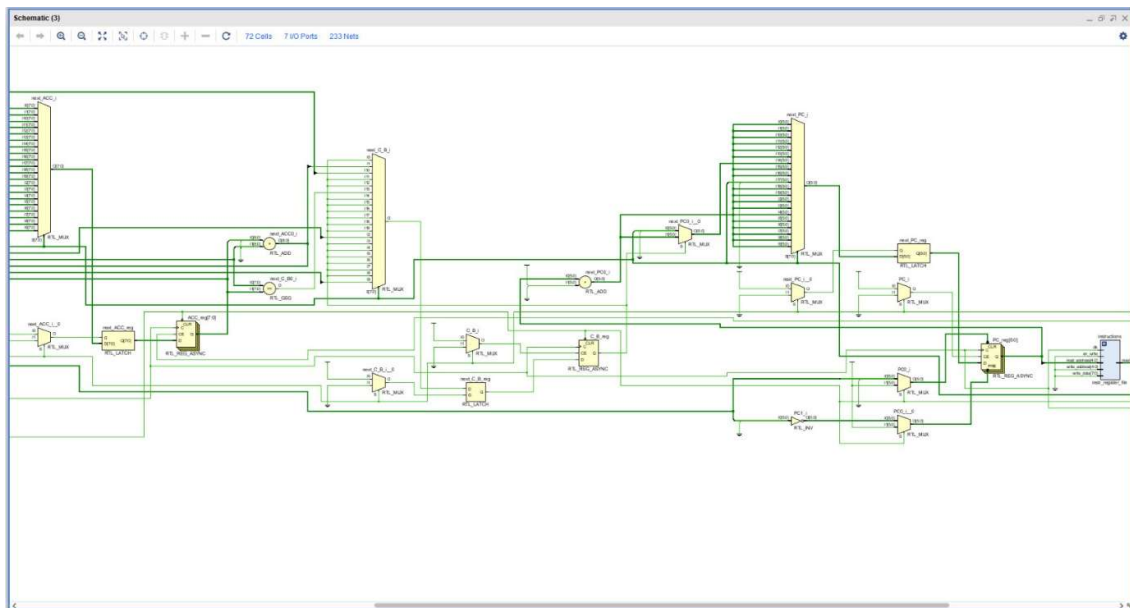

**Synthesis Schematic:**



